

CS2006: 計算機組織

Computer Arithmetic




Outline

- ◆ **Constructing an arithmetic logic unit (Appendix C)**
- ◆ **Multiplication (Sec. 3.3, Appendix C)**
- ◆ **Division (Sec. 3.4)**
- ◆ **Floating point (Sec. 3.5)**

Problem: Designing MIPS ALU

- ◆ Requirements: must support the following arithmetic and logic operations
 - **add, sub**: two's complement adder/subtractor with overflow detection
 - **and, or, nor** : logical AND, logical OR, logical NOR
 - **slt** (set on less than): two's complement adder with inverter, check sign bit of result

Functional Specification

 

ALU Control (ALUop)

0000

0001

0010

0110

0111

1100

Function

and

or

add

subtract

set-on-less-than

nor


A Bit-slice ALU

◆ Design trick 1: divide and conquer

32-bit ALU $\rightarrow$ 32 $\times$ 1-bit ALU


- Break the problem into simpler problems, solve them and glue together the solution

 ◆ Design trick 2: solve part of the problem and extend




A 1-bit ALU

 - ◆ Design trick 3: take pieces you know (or can imagine) and try to put them together




A 4-bit ALU

1-bit ALU

 


4-bit ALU

 

How about Subtraction?


- ◆ 2's complement: take inverse of every bit and add 1 (at c_{in} of first stage)

 - $A - B = A + (-B) = A + (B' + 1) = A + B' + 1$
- Bitwise inverse of B is B'




Revised Diagram

 - ◆ LSB and MSB need to do a little extra



Functional Specification

 

ALU Control (ALUop)

0000

0001

0010

0110

0111

1100

Function

✓ and

✓ or

✓ add

✓ subtract


set-on-less-than

nor


NOR Operation

DeMorgan's Theorem

 - ◆ $A \text{ nor } B = \text{not} (A \text{ or } B) = (\text{not } A) \text{ and } (\text{not } B)$



Functional Specification

 

ALU Control (ALUOp)

0000

0001

0010

0110

0111

1100

Function

and

or

add

subtract

set-on-less-than

nor

Overflow

Decimal	Binary	Decimal	2's complement
0	0000	0	0000
1	0001	-1	1111
2	0010	-2	1110
3	0011	-3	1101
4	0100	-4	1100
5	0101	-5	1011
6	0110	-6	1010
7	0111	-7	1001
		-8	1000

Ex: $7 + 3 = 10$ but ...

$$\begin{array}{r}
 \begin{array}{ccccccc}
 0 & 1 & 1 & 1 & & & \\
 \swarrow & \swarrow & \swarrow & \swarrow & & & \\
 0 & 0 & 1 & 1 & 1 & 1 & 7 \\
 + & 0 & 0 & 1 & 1 & & 3 \\
 \hline
 & 1 & 0 & 1 & 0 & & -6
 \end{array}
 \end{array}$$

$-4 - 5 = -9$ but ...

$$\begin{array}{r}
 \begin{array}{ccccccc}
 1 & 0 & 0 & 0 & & & \\
 \swarrow & \swarrow & \swarrow & \swarrow & & & \\
 1 & 1 & 1 & 0 & 0 & 0 & -4 \\
 + & 1 & 0 & 1 & 1 & & -5 \\
 \hline
 & 0 & 1 & 1 & 1 & & 7
 \end{array}
 \end{array}$$

Overflow Detection


- ◆ **Overflow: result too big/small to represent**
 - $-8 \leq 4\text{-bit binary number} \leq 7$
 - When adding operands with different signs, overflow will not occur!
 - Overflow occurs when adding:
 - 2 positive numbers and the sum is negative
 - 2 negative numbers and the sum is positive $\Rightarrow$ sign bit is set with the value of the result
 - Overflow if: **CarryIn of MSB $\neq$ CarryOut of MSB**

Diagram illustrating a carry chain in a ripple-carry adder. The inputs are 0111 (7) and 0011 (3). The sum is 1010 (-6). A red box highlights the first two bits of the first input (0 and 1), with arrows indicating the carry propagating through the second and third bits of both inputs.


Diagram illustrating a 5-bit ripple-carry adder. The inputs are 1000 and 1111. The sum is 0111 (7) and the carry-out is 1 (-4).

Overflow Detection Logic

 - ◆ **Overflow = CarryIn[N-1] XOR CarryOut[N-1]**



X	Y	X XOR Y
0	0	0
0	1	1
1	0	1
1	1	0

 


Dealing with Overflow

↗ for professionals

- ◆ Some languages (ex: C) ignore overflow
 - Use MIPS addu, addui, subu instructions
- ◆ Other languages (ex: Ada, Fortran) require raising an exception
 - 科學用途
 - Use MIPS add, addi, sub instructions
 - On overflow, invoke exception handler
 - Save PC in exception program counter (EPC) register
 - Jump to predefined handler address
 - mfc0 (move from coprocessor reg) instruction can retrieve EPC value, to return after corrective action

Functional Specification

 

ALU Control (ALUop)

0000

0001

0010

0110

0111

1100

Function

and

or

add


subtract

set-on-less-than

nor

Zero Detection Logic

 - Zero Detection Logic is a one BIG NOR gate (support conditional jump)



all bits zero $\Rightarrow$ \$Zero = 1
otherwise, \$Zero = 0

Functional Specification

 


Fig. B.5.14

ALU Control (ALUop)

0000

0001

0010

0110

0111

1100

Function

✓ and

✓ or

✓ add

✓ subtract

set-on-less-than

✓ nor

Fig. B.5.13

Set on Less Than (1/3)

$sle \$rd, \$rs, \$rt$ # $\$rs < \$rt, \$rd = 1$
 $\$rs \geq \$rt, \$rd = 0$
 ↓
 [LSB]

$\$rd = \begin{cases} 0, 0, \dots, 0, 1 \\ 0, 0, \dots, 0, 0 \end{cases}$

◆ 1-bit in ALU (for bits 1-30)


 


Fig. B.5.10a


Set on Less Than (2/3)

◆ Bit 31 in ALU

 

Set on Less Than (3/3)


◆ Bit 0 in ALU

 

Is that all for set-on-less-than? CarryOut

Also need to deal with overflow!
(但沒太重要, 我們重點是理解架構)


ALU Control and Function

 

ALU Control (ALUop)	Function
0000	and
0001	or
0010	add
0110	subtract
0111	set-on-less-than
1100	nor

OP₃ OP₂ OP₁ OP₀

Final 32-bit ALU

 

ALUop	Function
0000	and
0001	or
0010	add
0110	subtract
0111	set-on-less-than
1100	nor

Ripple Carry Adder



- ◆ Carry Ripple from lower-bit to the higher-bit

$$\begin{array}{r} 00111111 \\ \swarrow \swarrow \swarrow \swarrow \swarrow \swarrow \swarrow \swarrow \\ 00101010 \\ + 00010101 \leftarrow C_{in} = 1 \\ \hline 00000000 \end{array}$$

- ◆ Ripple computation dominates the run time
 - Higher-bit ALU must wait for carry from lower-bit ALU
 - Run time complexity: $O(n)$

  Problems with Ripple Carry Adder


- ◆ Carry bit may have to propagate from LSB to MSB => worst case delay: N-stage delay



Design Trick: look for parallelism and throw hardware at it


Remove the Dependency

◆ Ripple carry adder

 



◆ Carry lookahead adder

 - No carry bit propagation from LSB to MSB



Carry Lookahead: Theory (I)

(Appendix C.6)

  

◆ $\text{CarryOut} = (A * B) + (A * \text{CarryIn}) + (B * \text{CarryIn})$

- $\text{Cin}_2 = \text{Cout}_1 = (A_1 * B_1) + (A_1 * \text{Cin}_1) + (B_1 * \text{Cin}_1)$

- $\text{Cin}_1 = \text{Cout}_0 = (A_0 * B_0) + (A_0 * \text{Cin}_0) + (B_0 * \text{Cin}_0)$

◆ Substituting Cin₁ into Cin₂:

- $$\begin{aligned} \text{Cin}_2 &= (A_1 * B_1) + (A_1 * A_0 * B_0) + (A_1 * A_0 * \text{Cin}_0) + (A_1 * B_0 * \text{Cin}_0) \\ &\quad + (B_1 * A_0 * B_0) + (B_1 * A_0 * \text{Cin}_0) + (B_1 * B_0 * \text{Cin}_0) \\ &= (A_1 * B_1) + (A_1 + B_1) * (A_0 * B_0) + (A_1 + B_1) * (A_0 + B_0) * \text{Cin}_0 \end{aligned}$$

Carry Lookahead: Theory (II)

◆ Now define two new terms:

- Generate Carry at Bit i: $g_i = A_i * B_i$
- Propagate Carry via Bit i: $p_i = A_i + B_i$


◆ We can rewrite:

- $Cin_1 = g_0 + (p_0 * Cin_0)$
- $Cin_2 = g_1 + (p_1 * g_0) + (p_1 * p_0 * Cin_0)$
- $Cin_3 = g_2 + (p_2 * g_1) + (p_2 * p_1 * g_0) + (p_2 * p_1 * p_0 * Cin_0)$
- $Cin_4 = g_3 + (p_3 * g_2) + (p_3 * p_2 * g_1) + (p_3 * p_2 * p_1 * g_0) + (p_3 * p_2 * p_1 * p_0 * Cin_0)$


◆ Carry going into bit 3 is 1 if

- We generate a carry at bit 2 (g_2)
- Or we generate a carry at bit 1 (g_1) and bit 2 allows it to propagate ($p_2 * g_1$)
- Or we generate a carry at bit 0 (g_0) and bit 1 as well as bit 2 allows it to propagate ...
- Or the carry in (Cin_0) is 1 and all three bits (bit 0 to bit 2) allow it to propagate

 A Plumbing Analogy for Carry Lookahead (1, 2, 4 bits)




Carry Lookahead Unit

 

Common Carry Lookahead Adder

 
- ◆ Expensive to build a "full" carry lookahead adder
 - Just imagine length of the equation for $C_{in_{31}}$
- ◆ Common practices:
 - Cascaded carry look-ahead adder ← 數位系統設計
 - Multiple level carry look-ahead adder



Cascaded Carry Lookahead


- ◆ **Connects several N-bit lookahead adders to form a big one**

p, q, c_0 : initial input

 

Multiple Level Carry Lookahead

 - ◆ View an N-bit lookahead adder as a block
- ◆ Where to get C_{in} of the block ?




- Generate "super" P_i and G_i of the block
- Use next level carry lookahead structure to generate block C_{in}

Recap of Carry Lookahead Theory

◆ Now define two new terms:

 - Generate Carry at Bit i: $g_i = A_i * B_i$
- Propagate Carry via Bit i: $p_i = A_i + B_i$




◆ We can rewrite:


- $Cin_1 = g_0 + (p_0 * Cin_0)$
- $Cin_2 = g_1 + (p_1 * g_0) + (p_1 * p_0 * Cin_0)$
- $Cin_3 = g_2 + (p_2 * g_1) + (p_2 * p_1 * g_0) + (p_2 * p_1 * p_0 * Cin_0)$
- $Cin_4 = g_3 + (p_3 * g_2) + (p_3 * p_2 * g_1) + (p_3 * p_2 * p_1 * g_0) + (p_3 * p_2 * p_1 * p_0 * Cin_0) = G + (P * Cin_0)$

- **G: CarryOut can be generated among these 4 bits**
 - $G = g_3 + (p_3 * g_2) + (p_3 * p_2 * g_1) + (p_3 * p_2 * p_1 * g_0)$
- **P: CarryOut can be propagated among these 4 bits**
 - $P = p_3 * p_2 * p_1 * p_0$ 即 bit 0-3 的 A_i, B_i 至少有一个是 1.


Carry Lookahead Unit

 

Multiple Level Carry Lookahead

 

A Carry Lookahead Adder

 

A	B	Cout	
0	0	0	kill
0	1	Cin	propagate
1	0	Cin	propagate
1	1	1	generate


$$G = A * B$$

$$P = A + B$$

Fig. B.6.3


Carry-select Adder

$$CP(2n) = 2 * CP(n)$$

 

$$CP(2n) = CP(n) + CP(\text{mux})$$

只多了 2 to 1 mux 的 delay

 

Design trick: guess


Arithmetic for Multimedia

- ◆ Graphics and media processing operates on vectors of 8-bit and 16-bit data
 - Use 64-bit adder, with partitioned carry chain 分段 for 平行化
 - Operate on 8×8-bit, 4×16-bit, or 2×32-bit vectors
 - SIMD (single-instruction, multiple-data)
- ◆ Saturating operations
 - On overflow, result is largest representable value
 - c.f. 2s-complement modulo arithmetic
 - Ex: clipping in audio, saturation in video

Outline

- ◆ Constructing an arithmetic logic unit (Appendix C)
- ◆ Multiplication (Sec. 3.3, Appendix C)
- ◆ Division (Sec. 3.4)
- ◆ Floating point (Sec. 3.5)

MIPS R2000 Organization

 

Multiplication in MIPS

`mult $t1, $t2` `# t1 * t2`

- ◆ No destination register: product could be $\sim 2^{64}$; need two special registers to hold it
- ◆ 3-step process:

`$t1` `01111111111111111111111111111111`

`X $t2` `01000000000000000000000000000000`

`00011111111111111111111111111111` | `11000000000000000000000000000000`

HI

LO

`mfhi $t3`

`$t3` `00011111111111111111111111111111`

`mflo $t4`

`$t4` `11000000000000000000000000000000`

MIPS Multiplication

- ◆ Two 32-bit registers for product
 - HI: most-significant 32 bits
 - LO: least-significant 32 bits
- ◆ Instructions
 - `mult rs, rt` / `multu rs, rt`
 - 64-bit product in HI/LO
 - `mfhi rd` / `mflo rd`
 - Move from HI/LO to rd
 - Can test HI value to see if product overflows 32 bits
 - `mul rd, rs, rt` $\rightarrow$ $\begin{cases} \text{mult } \$rs, \$rt \\ \text{mflo } \$rd \end{cases}$ (高位元被丢掉!)
 - Least-significant 32 bits of product $\rightarrow$ rd

Unsigned Multiplication

- ♦ Paper and pencil example (unsigned):

Multiplicand
Multiplier

$$\begin{array}{r} 1000 \\ \times 1001 \\ \hline 1000 \\ 0000 \\ 0000 \\ 1000 \\ \hline 01001000 \end{array}$$


*add all
partial products*

Product


- ♦ m bits $\times$ n bits = $m+n$ bit product
- ♦ Binary makes it easy:
 - 0 $\Rightarrow$ place 0 ($0 \times$ multiplicand)
 - 1 $\Rightarrow$ place a copy ($1 \times$ multiplicand)
- ♦ 2 versions of multiply hardware and algorithm

Unsigned Multiplier (Ver. 1)

 - ◆ 64-bit *multiplicand* register (with 32-bit multiplicand at right half), 64-bit ALU, 64-bit *product* register, 32-bit *multiplier* register



Multiplication Algorithm (Ver. 1)

 

0010 x 1011


Product	Multiplier	Multiplicand
0000 0000	101 1	0000 0010
0000 0010	010 1	0000 0100
0000 0110	001 0	0000 1000
0000 0110	000 1	0001 0000
0001 0110	0000	0010 0000

Observations: Multiplier Ver. 1


- ◆ 1 clock per cycle → ~100 clocks per multiply
 - Ratio of multiply to add 5:1 to 100:1 比加减法慢很多.
- ◆ Half of the bits in multiplicand always 0
→ 64-bit adder is wasted
- ◆ 0's inserted in right of multiplicand as shifted
→ least significant bits of product never changed once formed
- ◆ Instead of shifting multiplicand to left, shift product to right?
- ◆ Product register wastes space → combine Multiplier and Product register

Unsigned Multiplier (Ver. 2)

 - ◆ 32-bit Multiplicand register, 32-bit ALU, 64-bit Product register (HI & LO in MIPS), (0-bit Multiplier register)



Multiplication Algorithm (Ver. 2)

 

0010 x 1011

Multiplicand	Product
0010	0000 1011
0010	0010 1011
0010	0001 0101
0010	0011 0101
0010	0001 1010
0010	0000 1101
0010	0010 1101
0010	0001 0110

Observations: Multiplier Ver. 2

- ◆ 2 steps per bit because multiplier and product registers combined
- ◆ MIPS registers HI and LO are left and right half of Product register
→ this gives the MIPS instruction MultU
- ◆ What about signed multiplication?
 - The easiest solution is to make both positive and remember whether to complement product when done (leave out sign bit, run for 31 steps)
 - Apply definition of 2's complement
 - sign-extend partial products and subtract at end
 - Booth's Algorithm is an elegant way to multiply signed numbers using same hardware as before and save cycles

Signed Multiplication

- ◆ Paper and pencil example (signed):

Multiplicand	1001 (-7)
Multiplier	X 1001 (-7)
	11111001
	+ 0000000
	+ 000000
	- 11001
Product	00110001 (49)

- ◆ Rule 1: Multiplicand sign extended
- ◆ Rule 2: Sign bit (MSB) of Multiplier

- 0 => 0 × multiplicand
- 1 => -1 × multiplicand

- ◆ Why rule 2 ?

- $X = s x_{n-2} x_{n-3} \dots x_1 x_0$ (2's complement)

- $\text{Value}(X) = -1 \times s \times 2^{n-1} + x_{n-2} \times 2^{n-2} + \dots + x_0 \times 2^0$

Booth's Algorithm: Motivation

- ◆ Example: $2 \times 6 = 0010 \times 0110$: $6 = 2 + 4$

	0010	
x	0110	
+	0000	shift (0 in multiplier)
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0000	shift (0 in multiplier)
	00001100	

- ◆ Can get same result in more than one way:

$$6 = -2 + 8 \qquad 0110 = -00010 + 01000$$

- ◆ Basic idea: replace a string of 1s with an initial subtract on seeing the first 1 and add on seeing the last 1

	0010	
x	0110	
	0000	shift (0 in multiplier)
-	0010	sub (first 1 in multiplier)
	0000	shift (mid string of 1s)
+	0010	add (prior step had last 1)
	00001100	

Booth's Algorithm: Rationale

end of run		1 1 1 1 0		beginning of run		
		$+2^5$ 2^4 2^3 2^2 -2^1				
Current Bit to bit	right	Explanation	Example			Op
1	0	Begins run of 1s	0000111 <u>1</u> 000			sub
1	1	Middle run of 1s	00001 <u>11</u> 1000			none (sub / add cancel)
0	1	End of run of 1s	000 <u>01</u> 111000			add
0	0	Middle run of 0s	0 <u>00</u> 01111000			none

Originally for speed (when shift was faster than add)

◆ Why it works?

$$\begin{array}{r}
 -10 \\
 + 100000 \\
 \hline
 011110
 \end{array}$$

$$\begin{array}{r}
 -2 \\
 +32 \\
 \hline
 30
 \end{array}$$

unsigned 乘法: $\oplus$
 Booth's algorithm: $\oplus, \ominus$

Booth's Algorithm

1. Depending on the current and previous bits, do one of the following:
 - 00**: Middle of a string of 0s, no arithmetic op.
 - 01**: End of a string of 1s, so add multiplicand to the left half of the product
 - 10**: Beginning of a string of 1s, so subtract multiplicand from the left half of the product
 - 11**: Middle of a string of 1s, so no arithmetic op.
2. As in the previous algorithm, shift the Product register right (arithmetically) 1 bit

$$\begin{array}{cccc}
 0 & 1 & 1 & 0 \\
 \downarrow & \downarrow & \downarrow & \downarrow \\
 +2^3 & +2^2 & -2^1 & \times \\
 \text{''} & -2^2 & \text{''} & \\
 +8 & \text{''} & -2 &
 \end{array}$$

Booths Example (2 x 7)

0010 0111
(-2 = 1110)

Operation	Multiplicand	Product	next?
0. initial value	0010	0000 ^{HI} 0111 ^{LO} 0	10 -> sub
1a. P = P - m	1110	+1110	↑
		1110 0111 0	shift P (sign ext)
1b.	0010	<u>1</u> 111 0011 1	11 -> nop, shift
2.	0010	<u>1</u> 111 1001 1	11 -> nop, shift
3.	0010	<u>1</u> 111 1100 1	01 -> add
4a.	0010	+0010	
		0001 1100 1	shift
4b.	0010	0000 1110 0	done


Booths Example (2 x -3)

$-3 = -8 + 4 + 1$

Operation	Multiplicand	Product	next?
0. initial value	0010	0000 1101 0	10 -> sub
1a. $P = P - m$	1110	+1110	
		1110 1101 0	shift P (sign ext)
1b.	0010	<u>1</u> 111 0 110 1	01 -> add
	0010	+0010	
2a.		0001 0 110 1	shift P
2b.	0010	0000 10 11 0	10 -> sub
	1110	+1110	
3a.	0010	1110 10 11 0	shift
3b.	0010	<u>1</u> 111 010 1 1	11 -> nop
4a.		1111 010 1 1	shift
4b.	0010	<u>1</u> 111 1010 1	done

Faster Multiplier

 
- ◆ A combinational multiplier
- ◆ Use multiple adders
 - Cost/performance tradeoff



- ◆ Can be pipelined
 - Several multiplication performed in parallel

Wallace Tree Multiplier

 - ◆ Use carry save adders: three inputs and two outputs



save: 没有要往高位元传递,
只拿出来做 shift.



- ◆ 8 1-bit full adders
 - One full adder delay (no carry propagation)
- ◆ The last stage is performed by regular adder (sum + carry)
- ◆ What is the minimum delay for 16 x 16 multiplier ?

$$\lceil 16 \times \frac{2}{3} \rceil = 11 \rightarrow \lceil 11 \times \frac{2}{3} \rceil = 8 \rightarrow \lceil 8 \times \frac{2}{3} \rceil = 6$$



$$\rightarrow \lceil 6 \times \frac{2}{3} \rceil = 4 \rightarrow \lceil 4 \times \frac{2}{3} \rceil = 3 \rightarrow \lceil 3 \times \frac{2}{3} \rceil = 2$$

total: 65 1-bit full adder delay
+ 15 16-bit full adder
 $O(\log_{\frac{3}{2}} N)$

Ripple Carry Adder vs. Carry Save Adder

  

Ripple Carry Adder

  


Carry Save Adder

Outline

- ◆ Constructing an arithmetic logic unit (Appendix C)
- ◆ Multiplication (Sec. 3.3, Appendix C)
- ◆ Division (Sec. 3.4)
- ◆ Floating point (Sec. 3.5)

MIPS R2000 Organization

 

Division in MIPS *(all 32-bit)*

`div $t1, $t2           # t1 / t2`

- ◆ Quotient stored in LO, remainder in HI

`mflo $t3           #copy quotient to t3`

`mfhi $t4           #copy remainder to t4`

- ◆ 3-step process

- ◆ Unsigned division:

`divu $t1, $t2       # t1 / t2`

- Just like `div`, except now interpret `t1`, `t2` as unsigned integers instead of signed
- Answers are also unsigned, use `mfhi`, `mflo` to access
- ◆ No overflow or divide-by-0 checking
 - Software must perform checks if required

Division: Paper & Pencil

		1001	Quotient
Divisor	1000	$\overline{)1001010}$	Dividend
(8-bit)		$\underline{-1000}$	(8-bit)
		0010	
		0101	
		1010	
		$\underline{-1000}$	
		10	Remainder

- ◆ See how big a number can be subtracted, creating quotient bit on each step
- ◆ Binary
 - 0 => place 0 (0 × divisor)
 - 1 => place a copy (1 × divisor)
- ◆ Two versions of divide, successive refinement
- ◆ Both dividend and divisor are positive integers

Divider Hardware (Version 1)

- ◆ 64-bit *Divisor* register (initialized with 32-bit divisor in left half), 64-bit ALU, 64-bit *Remainder* register (initialized with 64-bit dividend), 32-bit *Quotient* register

 


Fig. 3.10

Division Algorithm (Version 1)

$\begin{array}{r} 7 \\ 2 \end{array}$	$\begin{array}{r} 0111 \\ 0010 \end{array}$	
Quot.	Divisor	Rem.
0000	00100000	00000111
		(x) $\rightarrow$ 11100111
		00000111
0000	00010000	00000111
		$\rightarrow$ 11110111
		00000111
0000	00001000	00000111
		$\rightarrow$ 11111111
		00000111
0000	00000100	00000111
		$\rightarrow$ 00000011
		00000011
0001		00000011
0001	00000010	00000011
		$\rightarrow$ 00000001
		00000001
0011		00000001
0011	00000001	00000001

 


Fig. 3.11

Observations: Divider Version 1

- ◆ Half of the bits in divisor register always 0
 - => 1/2 of 64-bit adder is wasted
 - => 1/2 of divisor is wasted
- ◆ Instead of shifting divisor to right, shift remainder to left?
- ◆ 1st step cannot produce a 1 in quotient bit (otherwise quotient is too big for the register)
 - => switch order to shift first and then subtract
 - => save 1 iteration
- ◆ Eliminate Quotient register by combining with Remainder register as shifted left

Divider Hardware (Version 2)

- ◆ 32-bit Divisor register, 32-bit ALU, 64-bit Remainder register, (0-bit Quotient register)


 


Fig. 3.13

Division Algorithm (Version 2)

Step	Remainder	Div.
0	0000 0111	0010
1.1	0000 1110	
1.2	1110 1110	
1.3b	<u>0001</u> 1100	
2.2	1111 1100	
2.3b	<u>0011</u> 1000	
3.2	0001 1000	
3.3a	<u>0011</u> 0001	
4.2	0001 0001	
4.3a	<u>0010</u> 0011	
	0001 0011	

 

Is it correct all the time?

若除数为32-bit, 会被 shift 掉

Solution: 多存几个 bit 即可

→ Kill the spy!

Signed Division Rules

本堂課不教,但這裡提概念

◆ Signed Divides:

- Remember signs, make positive, complement quotient and remainder if necessary
- Let Dividend and Remainder have same sign and negate Quotient if Divisor sign & Dividend sign disagree,
- Ex: $-7 \div 2 = -3$, remainder = -1
 $-7 \div -2 = 3$, remainder = -1
- Satisfy Dividend = Quotient x Divisor + Remainder


餘數的 sign 應與被除數的 sign 一致。

Observations: Multiplier and Divider

- ◆ Same hardware as multiply: just need ALU to add or subtract, and 64-bit register to shift left or shift right
- ◆ HI and LO registers in MIPS combine to act as 64-bit register for multiplication and division

Multiplier/Divider Hardware

 - ◆ 32-bit Multiplicand/Divisor register, 32-bit ALU, 64-bit Product/Remainder register, (0-bit Multiplier/Quotient register)



MIPS Multiplication/Division Summary

◆ Start multiply, divide


- **MULT** *rs, rt* $\text{HI-LO} = rs \times rt \text{ // 64-bit signed}$
- **MULTU** *rs, rt* $\text{HI-LO} = rs \times rt \text{ // 64-bit unsigned}$
- **DIV** *rs, rt* $\text{LO} = rs \div rt; \text{HI} = rs \% rt (\%: \text{mod})$
- **DIVU** *rs, rt* $\text{// 64-bit unsigned}$ *(same as above. LO:Q, HI:R)*

◆ Move result from multiply, divide

- **MFHI** *rd* $rd = \text{HI}$
- **MFLO** *rd* $rd = \text{LO}$

◆ Move to HI or LO

 - **MTHI** *rd* $\text{HI} = rd$
- **MTLO** *rd* $\text{LO} = rd$



Outline

- ◆ Constructing an arithmetic logic unit (Appendix C)
- ◆ Multiplication (Sec. 3.3, Appendix C)
- ◆ Division (Sec. 3.4)
- ◆ Floating point (Sec. 3.5)

Floating Point: Motivation

◆ What can be represented in N bits?

Unsigned	0	to	$2^n - 1$
2's Complement	-2^{n-1}	to	$2^{n-1} - 1$
1's Complement	$-2^{n-1} + 1$	to	$2^{n-1} - 1$
Excess M	$-M$	to	$2^n - M - 1$

◆ But, what about ...

- very large numbers?

9,349,398,989,787,762,244,859,087,678

- very small numbers?

0.0000000000000000000000000045691

- rationals $\frac{2}{3}$

- irrationals $\sqrt{2}$

- transcendentals e, π

Floating Point: Example

♦ Floating Point

- $A = 31.48$


- $3 \rightarrow 3 \times 10^1$
- $1 \rightarrow 1 \times 10^0$
- $4 \rightarrow 4 \times 10^{-1}$
- $8 \rightarrow 8 \times 10^{-2}$

♦ Scientific notation

- $A = 3.148 \times 10^1$


- $3 \rightarrow 3 \times 10^0 \times 10^1$
- $1 \rightarrow 1 \times 10^{-1} \times 10^1$
- $4 \rightarrow 4 \times 10^{-2} \times 10^1$
- $8 \rightarrow 8 \times 10^{-3} \times 10^1$

Scientific Notation: Decimal

 

- ◆ Normalized form: no leading 0s
(exactly one digit to left of decimal point)
- ◆ Alternatives to represent 0.0000000035
 - Normalized: 3.5×10^{-9}
 - Not normalized: 0.35×10^{-8} , 35.0×10^{-10}


Scientific Notation: Binary

 

- ◆ Computer arithmetic that supports it is called floating point, because the binary point is not fixed, as it is for integers
 - ◆ Normalized form: no leading 0s (exactly one digit to left of binary point)
 - ◆ Alternatives to represent $1/2^9 + 1/2^{12}$
 - Normalized: 1.001×2^{-9}
 - Not normalized: 0.1001×2^{-8} , 10.01×2^{-10}
- fixed point: IIII.RRRR
(fixed # of bits reserved for the integer & the fraction part)*

FP Representation

 - ◆ Normalized format: $\pm 1.\text{xxxxxxxxxx}_{\text{two}} \times 2^{\pm \text{yyyy}_{\text{two}}}$
- ◆ Want to put it into multiple words: 32 bits for *single-precision* and 64 bits for *double-precision*
- ◆ A simple single-precision representation:



S represents sign


Exponent represents y's

Fraction represents x's

- ◆ Represent numbers as small as $\sim 1.2 \times 10^{-38}$ to as large as $\sim 3.4 \times 10^{38}$

Double Precision Representation

- ◆ Next multiple of word size (64 bits)

 

- ◆ Double precision (vs. single precision)

- Represent numbers almost as small as $\sim 2.2 \times 10^{-308}$ to almost as large as $\sim 1.8 \times 10^{308}$
- But primary advantage is greater accuracy due to larger fraction

Single → double
exp 8 → 11
frac 23 → 52

重點在“precision”，
非能表達的範圍

IEEE 754 Standard (1/4)

- ◆ Regarding single precision, DP similar
- ◆ Sign bit:
 - 1 means negative
 - 0 means positive
- ◆ Fraction:
 - To pack more bits, leading 1 implicit for normalized numbers (hidden leading 1 bit)
 - 1 + 23 bits for single, 1 + 52 bits for double
 - always true: $0 \leq \text{Fraction} < 1$
(for normalized numbers)
- ◆ Note: 0 has no leading 1, so reserve exponent value 0 just for number 0

$$1. \overset{2^{-1}}{} \overset{2^{-2}}{} \overset{2^{-3}}{} \dots \overset{2^{-23}}{}$$

fraction

IEEE 754 Standard (2/4)

◆ Exponent:

- Need to represent positive and negative exponents
- Also want to compare FP numbers as if they were integers, to help in value comparisons
- How about using 2's complement to represent?
Ex: 1.0×2^{-1} versus $1.0 \times 2^{+1}$ ($1/2$ versus 2)

1/2

0	1111 1111	000 0000 0000 0000 0000 0000
---	-----------	------------------------------

2

0	0000 0001	000 0000 0000 0000 0000 0000
---	-----------	------------------------------

*If we use integer comparison for these two words,
we will conclude that $1/2 > 2!!! \Rightarrow$ biased notation*

Biased (Excess) Notation

◆ Biased 7

0000	-7
0001	-6
0010	-5
0011	-4
0100	-3
0101	-2
0110	-1
0111	0
1000	1
1001	2
1010	3
1011	4
1100	5
1101	6
1110	7
1111	8

對半切 $2^8 = 256 \rightarrow 128$.
為何 bias 是 127?
∴ 保留 0000 0000 和 1111 1111
給例外狀況
⇒ 對半切 127 (去頭尾)

IEEE 754 Standard (3/4)

- ◆ Instead, let notation 0000 0000 be most negative, and 1111 1111 be most positive
- ◆ Called biased notation, where bias is the number subtracted to get the real number
 - IEEE 754 uses bias of 127 for single precision: Subtract 127 from Exponent field to get actual value for exponent
 - 1023 is bias for double precision (1 ~ 2046)

$$126 - 127 = -1$$

1/2

0	0111 1110	000 0000 0000 0000 0000 0000
---	-----------	------------------------------

2


0	1000 0000	000 0000 0000 0000 0000 0000
---	-----------	------------------------------

$$128 - 127 = 1$$

We can use integer comparison for floating point comparison.

IEEE 754 Standard (4/4)

◆ Summary (single precision):

 

$$(-1)^S \times \underbrace{(1.\text{Fraction})}_{\text{significand}} \times 2^{(\text{Exponent}-127)}$$

◆ Double precision are same, except with exponent bias of 1023

Example: FP to Decimal

0	0110 1000	101 0101 0100 0011 0100 0010
---	-----------	------------------------------

- ◆ Sign: 0 => positive
- ◆ Exponent:
 - $0110\ 1000_{\text{two}} = 104_{\text{ten}}$
 - Bias adjustment: $104 - 127 = -23$
- ◆ Fraction:
 - $1 + 2^{-1} + 2^{-3} + 2^{-5} + 2^{-7} + 2^{-9} + 2^{-14} + 2^{-15} + 2^{-17} + 2^{-22}$
 $= 1.0 + 0.666115$
- ◆ Represents: $1.666115_{\text{ten}} \times 2^{-23} \approx 1.986 \times 10^{-7}$

Example 1: Decimal to FP

- ◆ Number = - 0.75
 - = - $0.11_{\text{two}} \times 2^0$ (scientific notation)
 - = - $1.1_{\text{two}} \times 2^{-1}$ (normalized scientific notation)

- ◆ Sign: negative $\Rightarrow$ 1

- ◆ Exponent:

- Bias adjustment: $-1 + 127 = 126$
- $126_{\text{ten}} = 0111\ 1110_{\text{two}}$

$$0.75 \times 2 = 1.5$$
$$0.5 \times 2 = 1$$

1	0111 1110	100 0000 0000 0000 0000
---	-----------	-------------------------

Example 2: Decimal to FP

◆ A more difficult case: representing $1/3$?

转换:
×2直到>1

$$\begin{aligned} &= 0.33333..._{10} = 0.0101010101..._2 \times 2^0 \\ &\xleftarrow{\text{转换: } \times 2 \text{ 直到 } > 1} = 1.0101010101..._2 \times 2^{-2} \end{aligned}$$

$$\begin{aligned} 0.333 \times 2 &= 0.666 \\ 0.666 \times 2 &= 1.333 \\ 0.333 \times 2 &= 0.666 \\ &\vdots \end{aligned}$$

- Sign: 0
- Exponent = $-2 + 127 = 125_{10} = 01111101_2$
- Fraction = 0101010101...

0	0111 1101	0101 0101 0101 0101 0101 010
---	-----------	------------------------------

Single-Precision Range

◆ Exponents 00000000 and 11111111 reserved

◆ Smallest value

- Exponent: 00000001

- ⇒ actual exponent = $1 - 127 = -126$

- Fraction: 000...00 ⇒ significand = 1.0

- $\pm 1.0 \times 2^{-126} \approx \pm 1.2 \times 10^{-38}$

◆ Largest value

- exponent: 11111110

- ⇒ actual exponent = $254 - 127 = +127$

- Fraction: 111...11 ⇒ significand ≈ 2.0

- $\pm 2.0 \times 2^{+127} \approx \pm 3.4 \times 10^{+38}$

1.111111 ≈ 2
↓ ↓
 $2^{-1} 2^{-2} \dots$ 等比級数

Double-Precision Range

- ◆ Exponents 0000...00 and 1111...11 reserved
- ◆ Smallest value
 - Exponent: 000000000001
 $\Rightarrow$ actual exponent = $1 - 1023 = -1022$
 - Fraction: 000...00 $\Rightarrow$ significand = 1.0
 - $\pm 1.0 \times 2^{-1022} \approx \pm 2.2 \times 10^{-308}$
- ◆ Largest value
 - Exponent: 111111111110
 $\Rightarrow$ actual exponent = $2046 - 1023 = +1023$
 - Fraction: 111...11 $\Rightarrow$ significand ≈ 2.0
 - $\pm 2.0 \times 2^{+1023} \approx \pm 1.8 \times 10^{+308}$

Floating-Point Precision

◆ Relative precision

- All fraction bits are significant
- Single-precision: approx 2^{-23}
 - Equivalent to $23 \times \log_{10} 2 \approx 23 \times 0.3 \approx 6$ decimal digits of precision
- Double-precision: approx 2^{-52}
 - Equivalent to $52 \times \log_{10} 2 \approx 52 \times 0.3 \approx 15$ decimal digits of precision

$$2^{-23} = 10^{-x}$$

↪ 取 floor!

◆ Why precision matters?

- Moon to Earth distance: 384,400 KM
 - Apollo Guidance Computer (1966~1975)

Angles are in single precision

Distances and velocities are in double precision

Elapsed time is in triple precision

https://en.wikipedia.org/wiki/Apollo_Guidance_Computer

Zero and Special Numbers

- ◆ What have we defined so far? (single precision)

<u>Exponent</u>	<u>Fraction</u>	<u>Object</u>
0	0	<u>???</u>
0	nonzero	<u>???</u>
1-254	anything	+/- floating-point
255	0	<u>???</u>
255	nonzero	<u>???</u>

Representation for 0

◆ Represent 0?

- Exponent: all zeroes $\rightarrow$ no hidden 1.
- Fraction: all zeroes, too
- What about sign?
- +0: 0 00000000 000000000000000000000000
- -0: 1 00000000 000000000000000000000000

◆ Why two zeroes?

- Helps in some limit comparisons

Special Numbers

- ◆ What have we defined so far? (single precision)

<u>Exponent</u>	<u>Fraction</u>	<u>Object</u>
0	0	0 (± 0)
0	nonzero	???
1-254	anything	+/- floating-point
255	0	???
255	nonzero	???

- ◆ Range:

$$1.0 \times 2^{-126} \approx 1.2 \times 10^{-38}$$

What if result too small? (>0 , $< 1.2 \times 10^{-38} \Rightarrow$ Underflow!)

$$(2 - 2^{-23}) \times 2^{127} \approx 3.4 \times 10^{38}$$

What if result too large? ($> 3.4 \times 10^{38} \Rightarrow$ Overflow!)

Gradual Underflow

- ◆ Represent denormalized numbers (denorms)
 - Exponent : all zeroes *no hidden 1!*
 - Fraction : non-zeroes
 - Allow a number to degrade in significance until it become 0 (gradual underflow)
- The smallest normalized number
 - $1.0000\ 0000\ 0000\ 0000\ 0000\ 000 \times 2^{-126}$
- The smallest de-normalized number
 - $0.0000\ 0000\ 0000\ 0000\ 0000\ 001 \times 2^{-126}$ $\approx 2^{-149}$

*1.001 × 10⁻¹²⁶ ÷ 2
 = 0.5005 × 10⁻¹²⁶ 怎麼表達?
 ⇒ 0.101 × 10⁻¹²⁶ (denorm)
 ∴ gradual underflow*

*↑
 2⁻²³*

Special Numbers

- ◆ What have we defined so far? (single precision)

Exponent

0

0

1-254

255

255

Fraction

0

nonzero

anything

0

nonzero

Object

0

denorm

+/- floating-point

???

???

Representation for +/- Infinity

- ◆ In FP, divide by zero should produce +/- infinity, not overflow
- ◆ Why?
 - OK to do further computations with infinity
Ex: $X/0 > Y$ may be a valid comparison
- ◆ IEEE 754 represents +/- infinity
 - Most positive exponent reserved for infinity
 - Fractions all zeroes

S	1111 1111	0000 0000 0000 0000 0000 000
---	-----------	------------------------------

Special Numbers (cont'd)

◆ What have we defined so far? (single-precision)

<u>Exponent</u>	<u>Fraction</u>	<u>Object</u>
0	0	0
0	nonzero	denom
1-254	anything	+/- fl. pt. #
255	0	+/- infinity
255	nonzero	<u>???</u>

2^{-149}
 2^{-126} ↑ 很多!
 2^{128}
 ↑
 $1 - \text{fraction} \times 2^{129}$

gradual overflow? ↗
 佔不到什麼便宜, 因為 exp 本來就在較小的項次上
 $1 - \text{fraction} \times 2^{+128} \approx 2^{129}$ (from 2^{128} , 沒增加多少)

Representation for Not a Number

- ◆ What do I get if I calculate $\text{sqrt}(-4.0)$ or $0/0$?
 - If infinity is not an error, these should not be either
 - They are called *Not a Number* (NaN)
 - Exponent = 255, fraction nonzero
- ◆ Why is this useful?
 - Hope NaNs help with debugging?
 - They contaminate: $\text{op}(\text{NaN}, X) = \text{NaN}$
 - OK if calculate but don't use it

Special Numbers (cont'd)

- ◆ What have we defined so far? (single-precision)

Exponent

0

0

1-254

255

255

Fraction

0

nonzero

anything

0

nonzero

Object

0


denom

+/- fl. pt. #

+/- infinity

NaN

 Range of Single-Precision Floating Point Number



Adapted from Prof. Tseng's Class Material

Decimal Addition

- ◆ $A = 3.71345 \times 10^2$, $B = 1.32 \times 10^{-4}$, Perform $A + B$

$$\begin{array}{r} 3.71345 \times 10^2 \\ + 0.00000132 \times 10^2 \\ \hline 3.71345132 \times 10^2 \end{array}$$

- ◆ $A = 3.71345 \times 10^2$
 - ◆ $B = 1.32 \times 10^{-4} = 0.00000132 \times 10^2$
 - ◆ $A + B = (3.71345 + 0.00000132) \times 10^2$
- Right shift 2 – (-4) bits

Floating-Point Addition

Basic addition algorithm:

(1) Align binary point : compute $Y_e - X_e$

- ◆ right shift the smaller number, say X_m , that many positions to form $X_m \times 2^{X_e - Y_e}$ *記得 hidden 1*

(2) Add mantissa: compute $X_m \times 2^{X_e - Y_e} + Y_m$

(3) Normalization & check for over/underflow if necessary:

- left shift result, decrement result exponent
- right shift result, increment result exponent
- check overflow or underflow during the shift

(4) Round the mantissa and renormalize if necessary


這裡不提 rounding strategies ∴ 沒太重要.

(ex. round to the nearest even)

以便統計學上公平

Floating-Point Addition Example

- ◆ Now consider a 4-digit binary example
 - $1.000_2 \times 2^{-1} + -1.110_2 \times 2^{-2}$ (0.5 + -0.4375)
- ◆ 1. Align binary points
 - Shift number with smaller exponent
 - $1.000_2 \times 2^{-1} + -0.111_2 \times 2^{-1}$
- ◆ 2. Add mantissa
 - $1.000_2 \times 2^{-1} + -0.111_2 \times 2^{-1} = 0.001_2 \times 2^{-1}$
- ◆ 3. Normalize result & check for over/underflow
 - $1.000_2 \times 2^{-4}$, with no over/underflow
- ◆ 4. Round and renormalize if necessary
 - $1.000_2 \times 2^{-4}$ (no change) = 0.0625

 

FP Adder Hardware

(FPU)
not in ALU

- ◆ Much more complex than integer adder
- ◆ Doing it in one clock cycle would take too long
 - Much longer than integer operations
 - Slower clock would penalize all instructions
- ◆ FP adder usually takes several cycles
 - Can be pipelined

Decimal Multiplication

- ◆ $A = 3.12 \times 10^2$, $B = 1.5 \times 10^{-4}$, Perform $A \times B$

$$\begin{array}{r} 3.12 \times 10^2 \\ \times 1.5 \times 10^{-4} \\ \hline 4.68 \times 10^{-2} \end{array}$$

- ◆ $A = 3.12 \times 10^2$
- ◆ $B = 1.5 \times 10^{-4}$
- ◆ $A \times B = (3.12 \times 1.5) \times 10^{(2+(-4))}$
(×) (+)

Floating-Point Multiplication

Basic multiplication algorithm

- (1) Add exponents of operands to get exponent of product
doubly biased exponent must be corrected:

$$X_e = 7$$

$$Y_e = -3 \quad X_e = 1111 \quad = 15 \quad = 7 + 8$$

$$\text{Excess } 8 \quad Y_e = 0101 \quad = 5 \quad = -3 + 8$$


$$10100 \quad 20 \quad 4 + 8 + 8$$

need extra subtraction step of the bias amount

 - (2) Multiplication of operand mantissa
(3) Normalize the product & check overflow or underflow during the shift
(4) Round the mantissa and renormalize if necessary
(5) Set the sign of product (sign A XOR sign B)


Floating-Point Multiplication Example

- ◆ Now consider a 4-digit binary example
 - $1.000_2 \times 2^{-1} \times -1.110_2 \times 2^{-2}$ (0.5×-0.4375)
- ◆ 1. Add exponents
 - Unbiased: $-1 + -2 = -3$ *$E + 127 = exp$*
 - Biased: $(-1 + 127) + (-2 + 127) = -3 + 254 - 127 = -3 + 127$
- ◆ 2. Multiply operand mantissa
 - $1.000_2 \times 1.110_2 = 1.110_2 \Rightarrow 1.110_2 \times 2^{-3}$
- ◆ 3. Normalize result & check for over/underflow
 - $1.110_2 \times 2^{-3}$ (no change) with no over/underflow
- ◆ 4. Round and renormalize if necessary
 - $1.110_2 \times 2^{-3}$ (no change)
- ◆ 5. Determine sign:
 - $-1.110_2 \times 2^{-3} = -0.21875$



Adapted from Prof. CTH

MIPS R2000 Organization

 

MIPS Floating Point

- ◆ Separate floating point instructions:
 - Single-precision: `add.s`, `sub.s`, `mul.s`, `div.s`
 - Double-precision: `add.d`, `sub.d`, `mul.d`, `div.d`
- ◆ FP part of the processor:
 - contains 32 32-bit registers: `$f0`, `$f1`, ...
 - most registers specified in `.s` and `.d` instruction refer to this set
 - separate load and store: `lwc1` and `swc1`
 - `c1`: coprocessor 1 (FPU)
 - Double Precision: by convention, even/odd pair (约定) contain one DP FP number: `$f0/$f1`, `$f2/$f3`
 - Instructions to move data between main processor and coprocessors:
 - `mfc0`, `mtc0`, `mfc1`, `mtc1`, etc.

Interpretation of Data

The BIG Picture

- ◆ Bits have no inherent meaning
 - Interpretation depends on the instructions applied
- ◆ Computer representations of numbers
 - Finite range and precision
 - Need to account for this in programs

Associativity

- ◆ Floating Point add, subtract associative?
 - Let $x = -1.5 \times 10^{38}$, $y = 1.5 \times 10^{38}$, $z = 1.0$
 - $(x+y)+z = (-1.5 \times 10^{38} + 1.5 \times 10^{38}) + 1.0 = 0.0 + 1.0 = 1.0$
 - $x+(y+z) = -1.5 \times 10^{38} + (1.5 \times 10^{38} + 1.0) = -1.5 \times 10^{38} + 1.5 \times 10^{38} = 0.0$
- ◆ Therefore, Floating Point add, subtract are **not** associative!
 - Why? FP result approximates real result!
 - Since 1.5×10^{38} is so much larger than 1.0 that $1.5 \times 10^{38} + 1.0$ in floating point representation is still 1.5×10^{38}

Associativity in Parallel Programming

- ◆ Parallel programs may interleave operations in unexpected orders
 - Assumptions of associativity may fail
- ◆ Need to validate parallel programs under varying degrees of parallelism

x86 FP Architecture

- ◆ Originally based on 8087 FP coprocessor
 - 8 × 80-bit extended-precision registers
 - Used as a push-down stack
 - Registers indexed from TOS: ST(0), ST(1), ...
- ◆ FP values are 32-bit or 64 in memory
 - Converted on load/store of memory operand
 - Integer operands can also be converted on load/store
- ◆ Very difficult to generate and optimize code
 - Result: poor FP performance

x86 FP Instructions

Data transfer	Arithmetic	Compare	Transcendental
F I LD mem/ST(i) F I ST P mem/ST(i) FLDPI FLD1 FLDZ	F I ADD P mem/ST(i) F I SUB R P mem/ST(i) F I MUL P mem/ST(i) F I DIV R P mem/ST(i) FSQRT FABS FRNDINT	F I COMP P F I UCOMP P FSTSW AX/mem	FPATAN F2XMI FCOS FPTAN FPREM FPSIN FYL2X

- ◆ Optional variations
 - **I**: integer operand
 - **P**: pop operand from stack
 - **R**: reverse operand order
 - But not all combinations allowed

Streaming SIMD Extension 2 (SSE2)

- ◆ Adds 4×128 -bit registers
 - Extended to 8 registers in AMD64/EM64T
- ◆ Can be used for multiple FP operands
 - 2×64 -bit double precision
 - 4×32 -bit single precision
 - Instructions operate on them simultaneously
 - Single-Instruction Multiple-Data (SIMD)
- ◆ Follow-up extensions: SSE3, SSE4, AVX, AVX-2, AVX-512

Right Shift and Division

- ◆ Left shift by i places multiplies an integer by 2^i
- ◆ Right shift divides by 2^i ?
 - Only for unsigned integers
- ◆ For signed integers
 - Arithmetic right shift: replicate the sign bit
 - e.g., $-5 / 4$
 - $11111011_2 \gg 2 = 11111110_2 = -2$
 - Rounds toward $-\infty$
 - c.f. $11111011_2 \ggg 2 = 00111110_2 = +62$

Who Cares About FP Accuracy?

- ◆ Important for scientific code
 - But for everyday consumer use?
 - "My bank balance is out by 0.0002¢!" ☹
- ◆ The Intel Pentium FDIV bug, 1994
 - Recall cost: USD \$500M
 - The market expects accuracy
 - See Colwell, *The Pentium Chronicles*

Concluding Remarks

- ◆ ISAs support arithmetic
 - Signed and unsigned integers
 - Floating-point approximation to reals
- ◆ Bounded range and precision
 - Operations can overflow and underflow
- ◆ MIPS ISA
 - Core instructions: 54 most frequently used
 - 100% of SPECINT, 97% of SPECFP
 - Other instructions: less frequent

Concluding Remarks

- ◆ ISAs support arithmetic
 - Signed and unsigned integers
 - Floating-point approximation to reals
- ◆ Bounded range and precision
 - Operations can overflow and underflow
- ◆ MIPS ISA
 - Core instructions: 54 most frequently used
 - 100% of SPECINT, 97% of SPECFP
 - Other instructions: less frequent